

P1. (10 points) Design the simplest SOP circuit that implements the following function (show all steps): $F(A,B,C)=\sum m(1,3,4,6,7)$.

Then draw the circuit diagram using only NAND gates.

P2. (10 points) Realize each of the following Boolean functions using:

- 1) a minimum number of NAND only,
- 2) a minimum number of NOR gates only.

- A) $(A'B)+(AB')$
- B) $(AB)+(A'B')$

P3. (20 points) A full adder is a circuit that adds three bits X, Y, Z together and returns two bits C and S to represent the total as a 2-bit binary number C S. C is the MSB and S is the LSB. For example, if X=1, Y=1, Z=0, the total should be 2, or 10_2 in binary. Hence C=1 and S=0.

- A) Write the truth tables for the functions C and S.
- B) Write the functions C and S in short hand notation using (i) minterms and (ii) maxterms.
- C) Write the functions C and S in canonical sum-of-products (SOP) and canonical product-of-sums (POS) forms.
- D) Obtain the simplest SOP expressions for the functions C and S and draw their respective circuit diagrams.

P4. (20 points) A logic circuit has four inputs (A, B, C, D) and one output (F). The output is a **logic 0** if and only if three or four of the inputs are 0; the output is a **logic 1** otherwise.

- A) Find and draw the truth table.
- B) Write the maxterms expression for $F(A,B,C,D)$.
- C) Using AND and OR gates, design a minimum logic circuit to realize F.
- D) What is the cost of this circuit in terms of the number of gates and inputs?

P5. (15 points) A logic circuit has three inputs P, Q, R and one output S. S is high (Logic 1) whenever $P=0$ or whenever $Q=R=1$.

- A) Derive the truth table for the above.
- B) Use Boolean algebra to derive the simplified expression from the canonical SOP form.
- C) Derive the logic circuit for the simplified Boolean expression.

P6. (10 points) Consider the truth table below, which has three inputs (X,Y,Z) and two outputs (M,N):

X	Y	Z	M	N
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- A) Write the functions M and N in short-hand notation using minterms and maxterms (4 points).
- B) Write the functions M and N in canonical SOP and canonical POS forms then obtain the simplest SOP expressions for both M and N (6 points).

P7. (10 points) Show how to implement a NOT function using: (a) 2-input NAND gates only, (b) 2-input NOR gates only. For part (a) and part (b), you should use a different way from what has been shown in class (connecting both terminals to the input signal). Hint: you are allowed to connect constant voltages (i.e., logic values 0 or 1) to the inputs of the logic gates.

P8. (5 points) Rewrite the following function in SOP form:

$$F(a,b,c,d,e) = (a+c')(a+d)(ab'c+e)$$