

P1. (15 points) A sequential circuit has 2 rising edge triggered flip-flops (outputs A and B), two inputs (X and Y) and one output Z. One of the flip-flops is D the other is JK. The logic expressions for this circuit are:

$$D_a = X' \cdot Y + X \cdot A$$

$$J_b = X' \cdot B + X' \cdot A$$

$$K_b = Y \cdot B$$

$$Z = X \cdot B$$


- Sketch the circuit diagram
- Construct the transition table
- Construct the state diagram

P2. (40 points) A counter has a special counting sequence: 0, 5, 7, 1, 0, 5, 7, 1, and so on. Design this counter with minimal number of states.

- (5 points) Draw the state diagram for the counter.
- (5 points) Construct the state-assigned table including the next state and output.
- (10 points) Draw the circuit diagram for the counter using D flip-flops.
- (10 points) Repeat (c) using T flip-flops.
- (10 points) Repeat (c) using JK flip-flops.

P3. (15 points) Use synchronous sequential circuit (SSC) analysis to reverse engineer the operation of the circuit shown below.

 - Is this a Mealy or Moore machine?
- Write the expressions for Next State and Output logic.
- Draw the state transition diagram.



P4. (10 points) Draw the state diagram for a Mealy state machine with two inputs (X and Y) and two outputs (Z1 and Z2). The two inputs represent a two-bit binary number (N). If the present value of N is greater than the previous value of N then $Z1=0$ and $Z2=1$. And if the present value of N is less than the previous value of N then $Z1=1$ and $Z2=0$. Otherwise $Z1=Z2=0$.

P5. (20 points) Convert each of the following FSMs (shown below) to an ASM chart.

