



CprE / ComS 583 Reconfigurable Computing

Prof. Joseph Zambreno
Department of Electrical and Computer Engineering
Iowa State University

Lecture #18 –VHDL for Synthesis I




Recap – N-bit Register with Reset

```

ENTITY regn IS
  GENERIC ( N : INTEGER := 16 );
  PORT ( D      : IN STD_LOGIC_VECTOR(N-1 DOWNTO 0);
        Resetn, Clock : IN STD_LOGIC;
        Q      : OUT STD_LOGIC_VECTOR(N-1 DOWNTO 0) );
END regn;

ARCHITECTURE Behavior OF regn IS
BEGIN
  PROCESS ( Resetn, Clock )
  BEGIN
    IF Resetn = '0' THEN
      Q <= (OTHERS => '0');
    ELSIF Clock'EVENT AND Clock = '1' THEN
      Q <= D;
    END IF;
  END PROCESS;
END Behavior;

```

 

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.3



Recap – 4:1 Multiplexer

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY mux4to1 IS
  PORT ( w0, w1, w2, w3 : IN  STD_LOGIC;
        s                : IN  STD_LOGIC_VECTOR(1 DOWNTO 0);
        f                : OUT  STD_LOGIC );
END mux4to1;

ARCHITECTURE dataflow OF mux4to1 IS
BEGIN
  WITH s SELECT
    f <= w0 WHEN "00",
        w1 WHEN "01",
        w2 WHEN "10",
        w3 WHEN OTHERS;
END dataflow;

```

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.2




Recap – 4-bit Up-Counter with Reset

```

ARCHITECTURE Behavior OF upcount IS
  SIGNAL Count : STD_LOGIC_VECTOR(3 DOWNTO 0);
BEGIN
  PROCESS ( Clock, Resetn )
  BEGIN
    IF Resetn = '0' THEN
      Count <= "0000";
    ELSIF (Clock'EVENT AND Clock = '1') THEN
      IF Enable = '1' THEN
        Count <= Count + 1;
      END IF;
    END IF;
  END PROCESS;
  Q <= Count;
END Behavior;

```

 

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.4



Design Exercise

- Design a simple 32-bit CPU
- Requirements
 - Three instruction types: load/store, register ALU, branch-if-equal
 - 8 32-bit registers
 - ALU operations: ADD, SUB, OR, XOR, AND, CMP
 - Memory operations: load word, store word
- Components
 - Instruction memory / decode
 - Register file
 - ALU
 - Data memory
 - Other control

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.5



Outline


- Recap
- Finite State Machines
 - Moore Machines
 - Mealy Machines
- FSMs in VHDL
- State Encoding
- Example Systems
 - Serial Adder
 - Arbiter Circuit

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.6

Structure of a Typical Digital System

 

October 23, 2007 CprE 583 – Reconfigurable Computing Lect-18.7

Execution Unit (Datapath)

- Provides all necessary resources and interconnects among them to perform specified task
- Examples of resources
 - Adders, multipliers, registers, memories, etc.

October 23, 2007 CprE 583 – Reconfigurable Computing Lect-18.8

Control Unit (Control)

- Controls data movements in operational circuit by switching multiplexers and enabling or disabling resources
- Follows some 'program' or schedule
- Often implemented as Finite State Machine or collection of Finite State Machines

October 23, 2007 CprE 583 – Reconfigurable Computing Lect-18.9


Finite State Machines (FSMs)

- Any circuit with memory is a Finite State Machine
 - Even computers can be viewed as huge FSMs
- Design of FSMs involves
 - Defining states
 - Defining transitions between states
 - Optimization / minimization
- Above approach is practical for small FSMs only

October 23, 2007 CprE 583 – Reconfigurable Computing Lect-18.10

Moore FSM

 
- Output is a function of present state only





October 23, 2007 CprE 583 – Reconfigurable Computing Lect-18.11

Mealy FSM

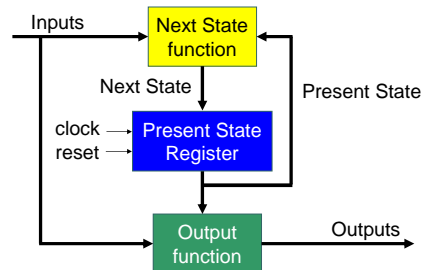- Output is a function of a present state and inputs





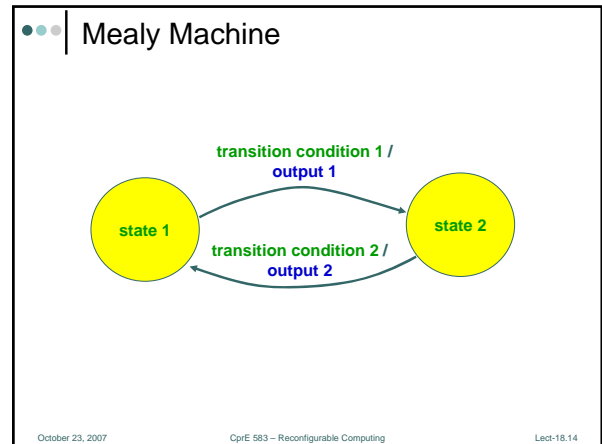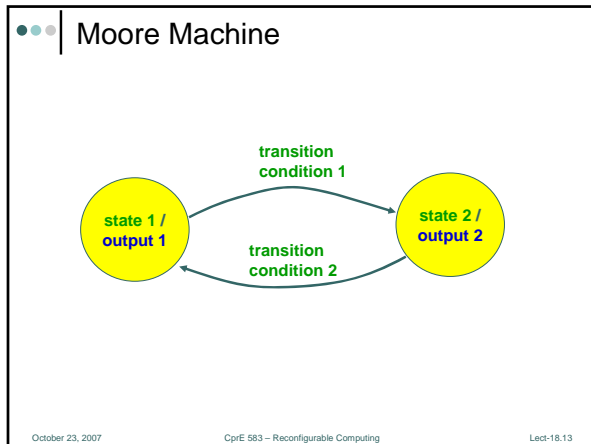October 23, 2007 CprE 583 – Reconfigurable Computing Lect-18.12




- ### Moore vs. Mealy FSM
- Moore and Mealy FSMs can be functionally equivalent
 - Equivalent Mealy FSM can be derived from Moore FSM and vice versa
 - Mealy FSM has richer description and usually requires smaller number of states
 - Smaller circuit area
- October 23, 2007 CprE 583 – Reconfigurable Computing Lect-18.15

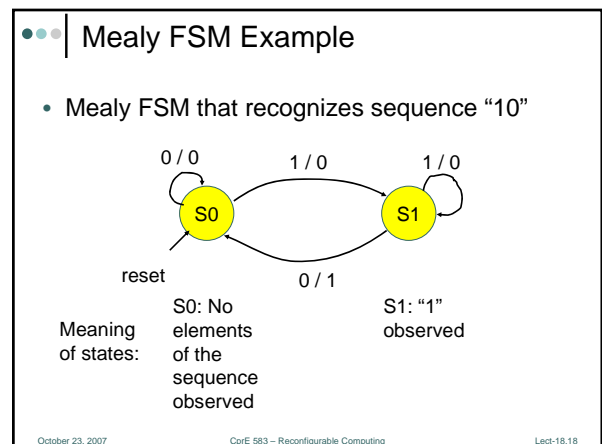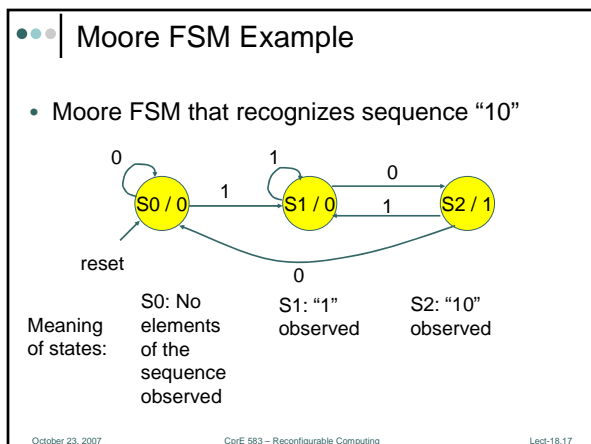- ### Moore vs. Mealy FSM (cont.)
- Mealy FSM computes outputs as soon as inputs change
 - Mealy FSM responds one clock cycle sooner than equivalent Moore FSM
 - Moore FSM has no combinational path between inputs and outputs
 - Moore FSM is more likely to have a shorter critical path
- October 23, 2007 CprE 583 – Reconfigurable Computing Lect-18.16



Mealy FSM Example (cont.)

 

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.19

FSMs in VHDL

- Finite State Machines can be easily described with processes
- Synthesis tools understand FSM description if certain rules are followed
 - State transitions should be described in a process sensitive to *clock* and *asynchronous reset* signals **only**
 - Outputs described as concurrent statements outside the process

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.20

Moore FSM Example – VHDL

```

TYPE state IS (S0, S1, S2);
SIGNAL Moore_state: state;

U_Moore: PROCESS (clock, reset)
BEGIN
    IF(reset = '1') THEN
        Moore_state <= S0;
    ELSIF (clock = '1' AND clock'event) THEN
        CASE Moore_state IS
            WHEN S0 =>
                IF input = '1' THEN
                    Moore_state <= S1;
                ELSE
                    Moore_state <= S0;
                END IF;
        
```

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.21

Moore FSM Example – VHDL (cont.)

```

            WHEN S1 =>
                IF input = '0' THEN
                    Moore_state <= S2;
                ELSE
                    Moore_state <= S1;
                END IF;
            WHEN S2 =>
                IF input = '0' THEN
                    Moore_state <= S0;
                ELSE
                    Moore_state <= S1;
                END IF;
        END CASE;
    END IF;
END PROCESS;

Output <= '1' WHEN Moore_state = S2 ELSE '0';

```

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.22

Mealy FSM Example – VHDL

```

TYPE state IS (S0, S1);
SIGNAL Mealy_state: state;

U_Mealy: PROCESS(clock, reset)
BEGIN
    IF(reset = '1') THEN
        Mealy_state <= S0;
    ELSIF (clock = '1' AND clock'event) THEN
        CASE Mealy_state IS
            WHEN S0 =>
                IF input = '1' THEN
                    Mealy_state <= S1;
                ELSE
                    Mealy_state <= S0;
                END IF;
        
```

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.23

Mealy FSM Example – VHDL (cont.)

```

            WHEN S1 =>
                IF input = '0' THEN
                    Mealy_state <= S0;
                ELSE
                    Mealy_state <= S1;
                END IF;
        END CASE;
    END IF;
END PROCESS;

Output <= '1' WHEN (Mealy_state = S1 AND input = '0') ELSE '0';

```

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.24

State Encoding Problem

- State encoding can have a big influence on optimality of the FSM implementation
 - No methods other than checking all possible encodings are known to produce optimal circuit
 - Feasible for small circuits only
- Using enumerated types for states in VHDL leaves encoding problem for synthesis tool

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.25

Types of State Encodings

- Binary (Sequential) – States encoded as consecutive binary numbers
 - Small number of used flip-flops
 - Potentially complex transition functions leading to slow implementations
- One-Hot – only one bit is active
 - Number of used flip-flops as big as number of states
 - Simple and fast transition functions
 - Preferable coding technique in FPGAs

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.26

Types of State Encodings (cont.)

State	Binary Code	One-Hot Code
S0	000	1000000
S1	001	0100000
S2	010	0010000
S3	011	0001000
S4	100	0000100
S5	101	0000010
S6	110	0000001
S7	111	0000000

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.27

Manual State Assignment

(ENTITY declaration not shown)

```

ARCHITECTURE Behavior OF simple IS
  TYPE State_type IS (A, B, C) ;
  ATTRIBUTE ENUM_ENCODING OF State_type      : STRING ;
  ATTRIBUTE ENUM_ENCODING OF State_type      : TYPE IS "00 01 11" ;
  SIGNAL y_present, y_next : State_type ;
BEGIN
cont ...

```

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.28

Manual State Assignment (cont.)

```

ARCHITECTURE Behavior OF simple IS
  SUBTYPE ABC_STATE is STD_LOGIC_VECTOR(1 DOWNTO 0);

  CONSTANT A : ABC_STATE := "00" ;
  CONSTANT B : ABC_STATE := "01" ;
  CONSTANT C : ABC_STATE := "11" ;

  SIGNAL y_present, y_next : ABC_STATE;
BEGIN
PROCESS ( w, y_present )
BEGIN
  CASE y_present IS
    WHEN A =>
      IF w = '0' THEN y_next <= A ;
      ELSE y_next <= B ;
      END IF ;
  ... cont


```

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.29


Serial Adder – Block Diagram

 

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.30

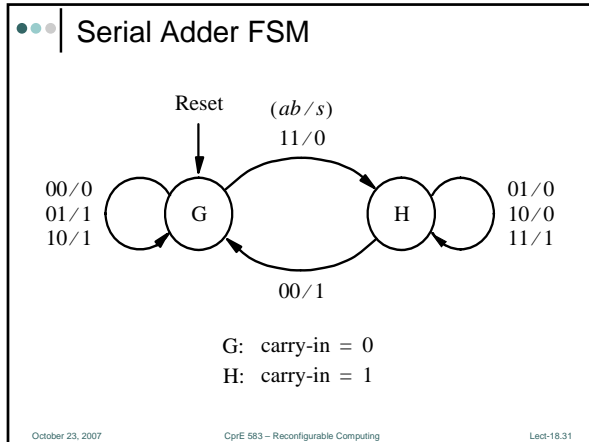

Serial Adder FSM – State Table

Present state	Next state				Output <i>s</i>			
	<i>ab</i> =00	01	10	11	00	01	10	11
G	G	G	H	H	0	1	1	0
H	G	H	H	H	1	0	0	1

October 23, 2007 CprE 583 – Reconfigurable Computing Lect-18.32

Serial Adder – Entity Declaration

```

1 LIBRARY ieee ;
2 USE ieee.std_logic_1164.all ;

3 ENTITY serial IS
4     GENERIC ( length : INTEGER := 8 ) ;
5     PORT ( Clock : IN STD_LOGIC ;
6           Reset : IN STD_LOGIC ;
7           A, B : IN STD_LOGIC_VECTOR(length-1 DOWNTO 0) ;
8           Sum : BUFFER STD_LOGIC_VECTOR(length-1 DOWNTO 0));
9 END serial ;

```

October 23, 2007 CprE 583 – Reconfigurable Computing Lect-18.33

Serial Adder – Architecture (2)

```

10 ARCHITECTURE Behavior OF serial IS
11     COMPONENT shiftrne
12     GENERIC ( N : INTEGER := 4 ) ;
13     PORT ( R : IN STD_LOGIC_VECTOR(N-1 DOWNTO 0) ;
14           L, E, w : IN STD_LOGIC ;
15           Clock : IN STD_LOGIC ;
16           Q : BUFFER STD_LOGIC_VECTOR(N-1 DOWNTO 0) ) ;
17     END COMPONENT ;

18 SIGNAL QA, QB, Null_in : STD_LOGIC_VECTOR(length-1 DOWNTO 0) ;
19 SIGNAL s, Low, High, Run : STD_LOGIC ;
20 SIGNAL Count : INTEGER RANGE 0 TO length ;

21 TYPE State_type IS ( G, H ) ;
22 SIGNAL y : State_type ;

```

October 23, 2007 CprE 583 – Reconfigurable Computing Lect-18.34

Serial Adder – Architecture (3)

```

23 BEGIN
24     Low <= '0' ; High <= '1' ;

25     ShiftA: shiftrne GENERIC MAP ( N => length)
26         PORT MAP ( A, Reset, High, Low, Clock, QA ) ;

27     ShiftB: shiftrne GENERIC MAP ( N => length)
28         PORT MAP ( B, Reset, High, Low, Clock, QB ) ;

```

October 23, 2007 CprE 583 – Reconfigurable Computing Lect-18.35

Serial Adder – Architecture (4)

```

29 AdderFSM: PROCESS ( Reset, Clock )
30 BEGIN
31     IF Reset = '1' THEN
32         y <= G ;
33     ELSIF Clock'EVENT AND Clock = '1' THEN
34         CASE y IS
35             WHEN G =>
36                 IF QA(0) = '1' AND QB(0) = '1' THEN y <= H ;
37                 ELSE y <= G ;
38             END IF ;
39             WHEN H =>
40                 IF QA(0) = '0' AND QB(0) = '0' THEN y <= G ;
41                 ELSE y <= H ;
42             END IF ;
43         END CASE ;
44     END IF ;
45 END PROCESS AdderFSM ;

```

October 23, 2007 CprE 583 – Reconfigurable Computing Lect-18.36

Serial Adder – Architecture (5)

```

46 WITH y SELECT
47   s <= QA(0) XOR QB(0) WHEN G,
48     NOT ( QA(0) XOR QB(0) ) WHEN H ;
49 Null_in <= (OTHERS => '0') ;
50 ShiftSum: shiftme GENERIC MAP ( N => length )
51   PORT MAP ( Null_in, Reset, Run, s, Clock, Sum ) ;

```

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.37

Serial Adder – Architecture (5)

```

52 Stop: PROCESS
53 BEGIN
54   WAIT UNTIL (Clock'EVENT AND Clock = '1') ;
55   IF Reset = '1' THEN
56     Count <= length ;
57   ELSIF Run = '1' THEN
58     Count <= Count -1 ;
59   END IF ;
60 END PROCESS ;
61 Run <= '0' WHEN Count = 0 ELSE '1' ; -- stops counter and ShiftSum
62 END Behavior ;


```

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.38

Serial Adder - Mealy FSM Circuit

 


October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.39

Arbiter Circuit

 


October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.40

Arbiter Moore State Diagram

 

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.41

Grant Signals – VHDL Code

```

.
.
.
PROCESS( y )
BEGIN
  g(1) <= '0' ;
  g(2) <= '0' ;
  g(3) <= '0' ;
  IF y = gnt1 THEN g(1) <= '1' ;
  ELSIF y = gnt2 THEN g(2) <= '1' ;
  ELSIF y = gnt3 THEN g(3) <= '1' ;
  END IF ;
END PROCESS ;
END Behavior ;


```

October 23, 2007

CprE 583 – Reconfigurable Computing

Lect-18.42

Arbiter Simulation Results

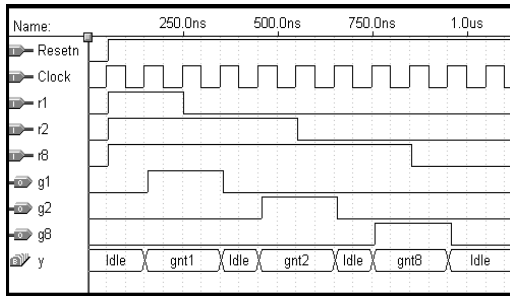

October 23, 2007

CprE 583 - Reconfigurable Computing

Lect-18.43